

Control Systems

G V V Sharma*

CONTENTS

1 Feedback Transconductance Amplifier: Series-Series	1
2 Feedback Voltage Amplifier: Series-Shunt	4
3 Feedback Current Amplifier: Shunt-Series	4
3.1 Ideal Case	4
3.2 Practical Case	4

Abstract—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/feedback/codes>

1 FEEDBACK TRANSCONDUCTANCE AMPLIFIER: SERIES-SERIES

1.0.1. draw the block diagram of a Feedback Transconductance Amplifier(series-series)

Solution: fig.1.0.1 gives us the required block diagram

$$T = \frac{I_o}{V_s} = \frac{G}{1 + GH} \quad (1.0.1.1)$$

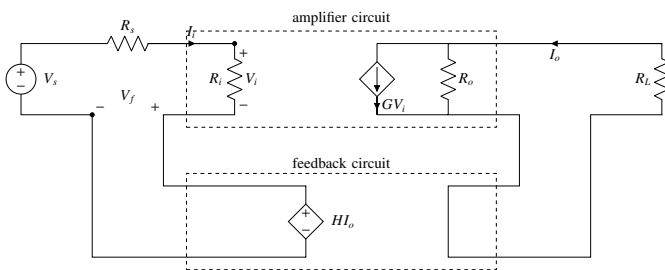


Fig. 1.0.1: Feedback Transconductance Amplifier

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

1.0.2. draw the equivalent amplifier circuit block diagram of fig.1.0.1

Solution: fig.1.0.2 gives the required block diagram

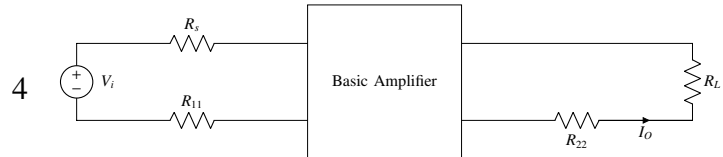


Fig. 1.0.2: Amplifier circuit block diagram

$$G = \frac{I_o}{V_i} \quad (1.0.2.1)$$

R_{11} and R_{22} are obtained from fig.1.0.2

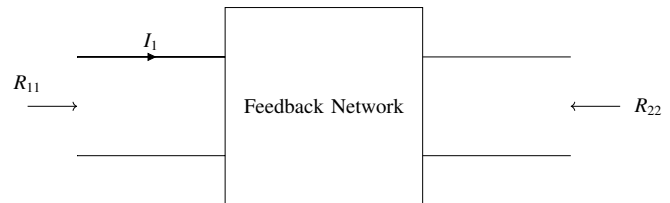


Fig. 1.0.2: feedback network

1.0.3. draw the equivalent feedback circuit block diagram of fig.1.0.1

Solution: fig.1.0.3 gives the required block diagram

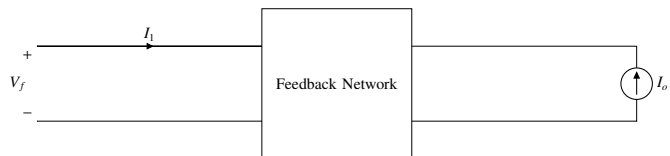


Fig. 1.0.3: Feedback circuit block diagram

$$H = \frac{V_f}{I_o} \bigg|_{I_i=0} \quad (1.0.3.1)$$

1.0.4. Part of the circuit of the MC1553 Amplifier is shown in circuit1 in fig.1.0.4 ,Answer below questions using equivalent block diagrams in fig.1.0.1 and values from Table 1.0.4

1.0.5. feedback analysis to find open loop gain G

Solution: employing equivalent amplifier block diagram fig.1.0.2 into circuit in fig.1.0.4, R_{11} and R_{22} are

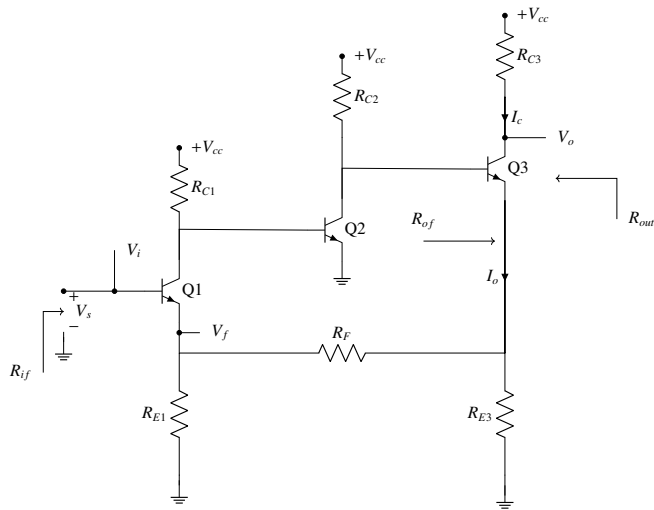


Fig. 1.0.4: circuit1

Parameter	Value
R_{C1}	$9k\Omega$
R_{E1}	100Ω
R_{C2}	$5k\Omega$
R_F	640Ω
R_{E2}	100Ω
R_{C3}	600Ω
h_{fe}	100
r_o	$\infty\Omega$
I_{C1}	0.6mA
I_{C2}	1mA
I_{C3}	4mA
r_{e1}	41.7Ω
$r_{\pi2}$	$2.5k\Omega$
α_1	0.99
g_{m2}	40mA/V
r_{e3}	6.25Ω
r_{o3}	$25k\Omega$
$r_{\pi3}$	625Ω

TABLE 1.0.4: parameters

found from feedback circuit in fig.1.0.4 using rule from fig.1.0.2 we finally obtain

$$R_s, R_L = 0 \quad (1.0.5.1)$$

$$R_{11} = R_{E1} \parallel (R_F + R_{E2}) \quad (1.0.5.2)$$

$$R_{22} = R_{E2} \parallel (R_F + R_{E1}) \quad (1.0.5.3)$$

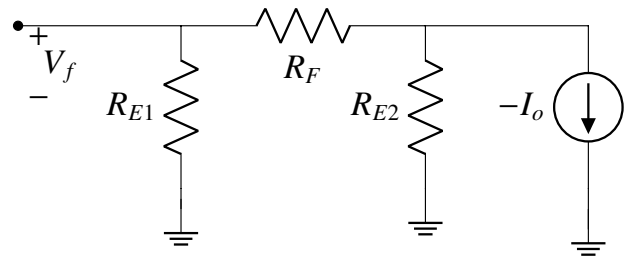


Fig. 1.0.4: H circuit

finally Amplifier circuit is obtained shown in fig.1.0.5

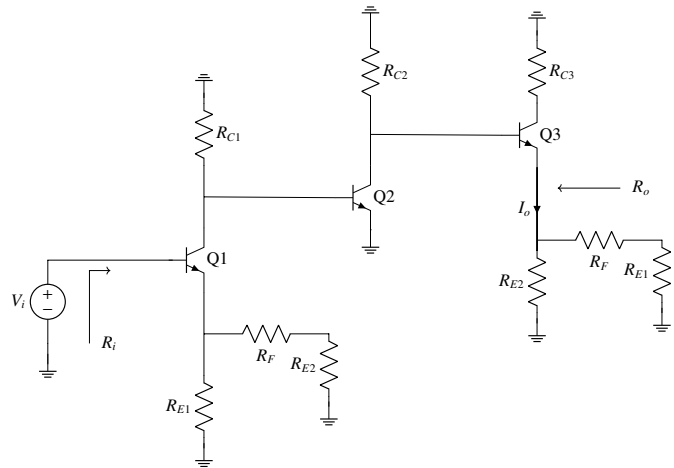


Fig. 1.0.5: G circuit

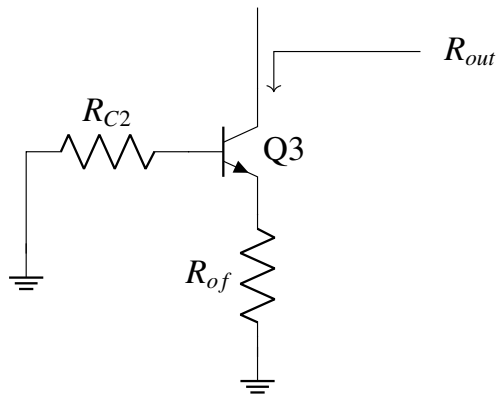


Fig. 1.0.5: circuit4

to find $G = \frac{I_o}{V_i}$ we determine the gain of first stage, this is written by inspection as-

$$\frac{V_{c1}}{V_i} = \frac{-\alpha(R_{C1} \parallel r_{\pi2})}{r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))} \quad (1.0.5.4)$$

using values from 1.0.4

$$\frac{V_{c1}}{V_i} = -14.92V/V \quad (1.0.5.5)$$

Next, we determine the gain of the second stage, which can be written by inspection (noting that $V_{b2} = V_{c1}$) as

$$\frac{V_{c2}}{V_{c1}} = -g_{m2}R_{c2}[(h_{fe} + 1)(r_{e3} + (R_{E2} \parallel (R_F + R_{E1})))] \quad (1.0.5.6)$$

substituting results in

$$\frac{V_{c2}}{V_{c1}} = -131.2V/V \quad (1.0.5.7)$$

Finally, for the third stage we can write by inspection

$$\frac{I_0}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} \parallel (R_F + R_{E1}))} \quad (1.0.5.8)$$

substituting values from 1.0.4 gives

$$\frac{I_0}{V_{c2}} = 10.6mA/V \quad (1.0.5.9)$$

combining the gains of the three stages results in

$$G = \frac{I_0}{V_i} = -14.92 \times -131.2 \times 10.6 \times 10^{-3} = 20.7A/V \quad (1.0.5.10)$$

1.0.6. Find Feedback Factor H

Solution: employing the equivalent feedback circuit block diagram we get H circuit in fig.1.0.4

$$H = \frac{V_f}{I_0} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \quad (1.0.6.1)$$

$$H = \frac{100}{100 + 640 + 100} \times 100 = 11.9\Omega \quad (1.0.6.2)$$

1.0.7. Find closed loop gain T and Voltage Gain V_0/V_s

Solution:

$$T = \frac{I_0}{V_s} = \frac{G}{1 + GH} = \frac{20.7}{1 + 20.7 \times 11.9} = 83.7mA/V \quad (1.0.7.1)$$

the voltage gain is found from

$$\frac{V_0}{V_s} = \frac{-I_c R_{c3}}{V_s} \approx \frac{-I_0 R_{c3}}{V_s} = -T R_{c3} \quad (1.0.7.2)$$

$$= -83.7 \times 10^{-3} \times 600 = -50.2V/V \quad (1.0.7.3)$$

1.0.8. Now assume Loop gain is large and find approximate expression for closed loop gain $T = \frac{I_0}{V_s}$

Solution: When $GH \gg 1$,

$$T = \frac{I_0}{V_s} \approx \frac{1}{H} \quad (1.0.8.1)$$

as

$$H = \frac{V_f}{I_0} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \quad (1.0.8.2)$$

$$= \frac{100}{100 + 640 + 100} \times 100 = 11.9\Omega \quad (1.0.8.3)$$

thus,

$$T = \frac{1}{11.9} = 84mA/V \quad (1.0.8.4)$$

$$\frac{I_c}{V_s} \approx \frac{I_0}{V_s} = 84mA/V \quad (1.0.8.5)$$

which we note is very close to the approximate value found in (1.0.7.1)

1.0.9. Find R_{in} and R_{out} for circuit in fig.1.0.4

Solution:

$$R_{in} = R_{if} = R_i(1 + GH) \quad (1.0.9.1)$$

where R_i is the input resistance of the G circuit. The value of R_i can be found from the circuit in fig.1.0.5 as follows:

$$R_i = (h_{fe} + 1)(r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))) = 13.65K\Omega \quad (1.0.9.2)$$

$$R_{if} = 13.65(1 + 20.7 \times 11.9) = 3.38M\Omega \quad (1.0.9.3)$$

$$R_{of} = R_o(1 + GH) \quad (1.0.9.4)$$

where R_o can be determined to be

$$R_o = (R_{E2} \parallel (R_F + R_{E1})) + r_{e3} + \frac{R_{C2}}{h_{fe} + 1} \quad (1.0.9.5)$$

from values in Table 1.0.4, yields $R_o = 143.9\Omega$. The output resistance R_{of} of the feedback amplifier can now be found as

$$R_{of} = R_o(1 + GH) = 143.9(1 + 20.7 \times 11.9) = 35.6K\Omega \quad (1.0.9.6)$$

R_{out} is found by using circuit4 in fig.1.0.5

$$R_{out} = r_{o3} + [R_{of} \parallel (r_{\pi3} + R_{C2})](1 + g_{m3}r_{o3} \frac{r_{\pi3}}{r_{\pi3} + R_{C2}}) \quad (1.0.9.7)$$

$$= 25 + [35.6 \parallel (5.625)][1 + 160 \times 25 \frac{0.625}{5.625}] = 2.19M\Omega \quad (1.0.9.8)$$

thus R_{out} is increased (from r_{o3}) but not by $(1+GH)$

1.0.10. put the obtained parameters in a table

Solution:

1.0.11. Represent this amplifier in a control system Block Diagram

Solution: figure in fig.1.0.11 represents our control system

1.0.12. write a code for doing calculations and verify the values obtained in 1.0.10

Solution: following code does all the calculations of above equations to give parameters in 1.0.10

```
codes/ee18btech11007/circuit_calc.py
```

Parameter	Value
G	20.7A/V
H	11.9Ω
T	83.7mA/V
V_o/V_s	-50.2V/V
R_{in}	$3.38M\Omega$
R_{out}	$2.19M\Omega$
R_{of}	$35.6k\Omega$

TABLE 1.0.10: parameters

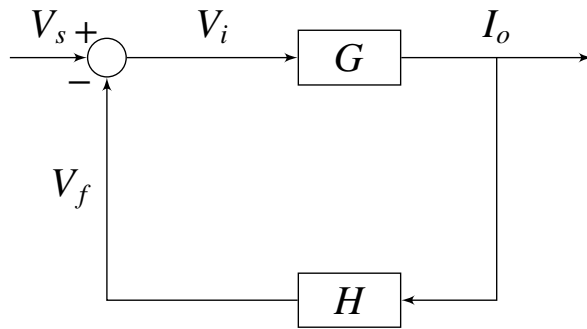


Fig. 1.0.11: block diagram

2 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

3 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

3.1 *Ideal Case*

3.2 *Practical Case*