

CONTENTS

1	Stability	1
2	Routh Hurwitz Criterion	1
3	Compensators	1
4	Nyquist Plot	1
5	Feedback systems	1

Abstract—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

1 STABILITY

2 ROUTH HURWITZ CRITERION

3 COMPENSATORS

4 NYQUIST PLOT

5 FEEDBACK SYSTEMS

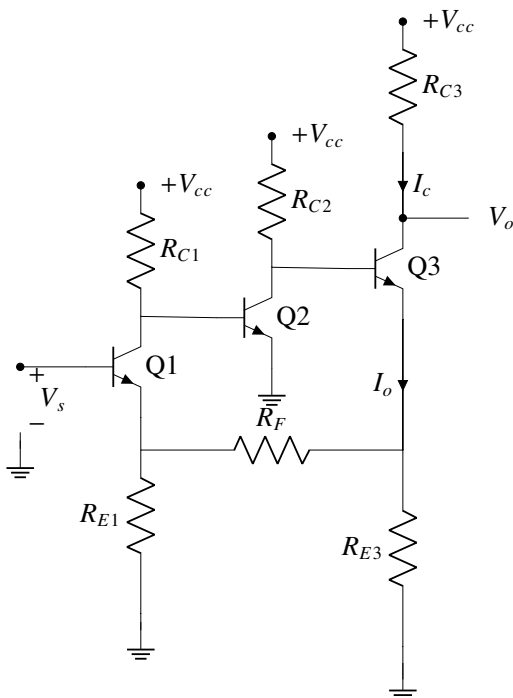


Fig. 5.0.0: circuit1

5.0.1. Part of the circuit of the MC1553 Amplifier is shown in circuit1 in fig.5.0.0 Assume the loop gain is large, find an approximate expression and value for the closed loop gain $A_f = \frac{I_0}{V_s}$ and

for $\frac{I_c}{V_s}$, take $R_{E1} = 100\Omega, R_{C1} = 9K\Omega, R_{C2} = 5K\Omega, R_F = 640\Omega, R_{E2} = 100\Omega, R_{C3} = 600\Omega, h_{fe} = 100, r_0 = \infty, I_{C1} = 0.6mA, I_{C2} = 1mA, I_{C3} = 4mA$

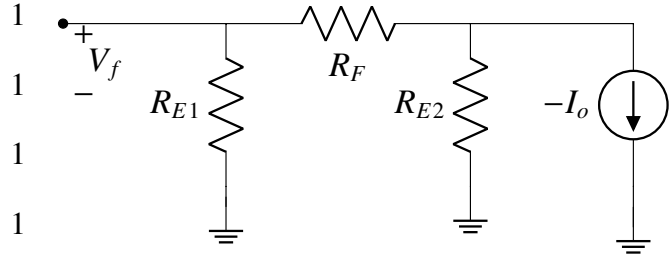


Fig. 5.0.1: circuit2

Solution: When $GH \gg 1$,

$$A_f = \frac{I_0}{V_s} \approx \frac{1}{H} \quad (5.0.1.1)$$

feedback factor H can be found from feedback network. The feedback network consists of resistors R_{E1}, R_F, R_{E2} using circuit2 in fig.5.0.1 we get

$$H = \frac{V_f}{I_0} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \quad (5.0.1.2)$$

$$= \frac{100}{100 + 640 + 100} \times 100 = 11.9\Omega \quad (5.0.1.3)$$

thus,

$$A_f \approx \frac{1}{H} \quad (5.0.1.4)$$

$$= \frac{1}{R_{E2}} \left(1 + \frac{R_{E2} + R_F}{R_{E1}} \right) \quad (5.0.1.5)$$

$$= \frac{1}{11.9} = 84mA/V \quad (5.0.1.6)$$

$$\frac{I_c}{V_s} \approx \frac{I_0}{V_s} = 84mA/V \quad (5.0.1.7)$$

5.0.2. Find $\frac{V_0}{V_s}$

Solution:

$$\frac{V_0}{V_s} = \frac{-I_c R_{C3}}{V_s} = -84 \times 0.6 = -50.4V/V \quad (5.0.2.1)$$

5.0.3. use feedback analysis to find G, H, A_f , $\frac{V_0}{V_s}$, R_{in} and R_{out} . for calculating R_{out} assume r_0 of Q_3 is $25k\Omega$

Solution: employing loading rules in fig.5.0.0, we obtain circuit3 given in fig.5.0.3

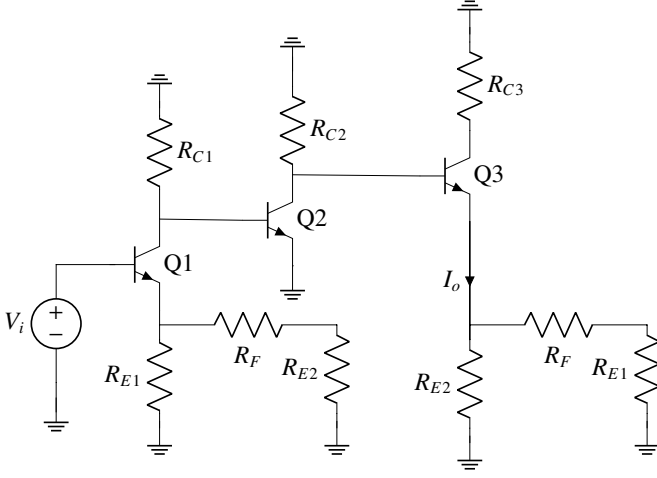


Fig. 5.0.3: circuit3

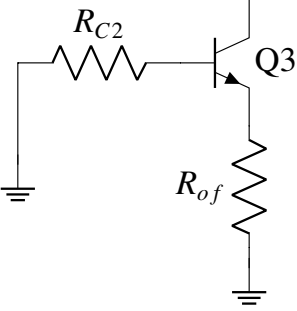


Fig. 5.0.3: circuit4

to find $G = \frac{I_o}{V_i}$ we determine the gain of first stage, this is written by inspection as-

$$\frac{V_{c1}}{V_i} = \frac{-\alpha(R_{c1} || r_{\pi 2})}{r_{e1} + (R_{E1} || (R_F + R_{E2}))} \quad (5.0.3.1)$$

Since Q_1 is biased at 0.6mA, $r_{e1} = 41.7\Omega$, Transistor Q_2 is biased at 1mA, thus

$$r_{\pi 2} = \frac{h_{fe}}{g_{m2}} = \frac{100}{40} = 2.5K\Omega. \quad (5.0.3.2)$$

Substituting these values together with $\alpha_1 = 0.99$, $R_{C1} = 9K\Omega$, $R_{E1} = 100\Omega$, $R_F = 640\Omega$, and $R_{E2} = 100\Omega$, results in

$$\frac{V_{c1}}{V_i} = -14.92V/V \quad (5.0.3.3)$$

Next, we determine the gain of the second stage, which can be written by inspection (noting that $V_{b2} = V_{c1}$) as

$$\frac{V_{c2}}{V_{c1}} = -g_{m2}R_{c2} || (h_{fe} + 1)[r_{e3} + (R_{E2} || (R_F + R_{E1}))] \quad (5.0.3.4)$$

substituting the values, results in

$$\frac{V_{c2}}{V_{c1}} = -131.2V/V \quad (5.0.3.5)$$

Finally, for the third stage we can write by inspection

$$\frac{I_o}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} || (R_F + R_{E1}))} \quad (5.0.3.6)$$

$$\frac{1}{6.25 + (100 || 740)} = 10.6mA/V \quad (5.0.3.7)$$

combining the gains of the three stages results in

$$G = \frac{I_o}{V_i} = -14.92 \times -131.2 \times 10.6 \times 10^{-3} = 20.7A/V \quad (5.0.3.8)$$

the closed loop gain A_f is found from

$$A_f = \frac{I_o}{V_s} = \frac{G}{1 + GH} = \frac{20.7}{1 + 20.7 \times 11.9} = 83.7mA/V \quad (5.0.3.9)$$

which we note is very close to the approximate value found in (5.0.1.7), above the voltage gain is found from

$$\frac{V_o}{V_s} = \frac{-I_o R_{c3}}{V_s} \approx \frac{-I_o R_{c3}}{V_s} = -A_f R_{c3} \quad (5.0.3.10)$$

$$= -83.7 \times 10^{-3} \times 600 = -50.2V/V \quad (5.0.3.11)$$

which is also very close to the approximate value found in (5.0.1.7) above given by

$$R_{in} = R_{if} = R_i(1 + GH) \quad (5.0.3.12)$$

where R_i is the input resistance of the G circuit. The value of R_i can be found from the circuit in fig. 5.0.3 as follows:

$$R_i = (h_{fe} + 1)(r_{e1} + (R_{E1} || (R_F + R_{E2}))) = 13.65K\Omega \quad (5.0.3.13)$$

$$R_{if} = 13.65(1 + 20.7 \times 11.9) = 3.38M\Omega \quad (5.0.3.14)$$

$$R_{of} = R_o(1 + GH) \quad (5.0.3.15)$$

where R_o can be determined to be

$$R_o = (R_{E2} || (R_F + R_{E1})) + r_{e3} + \frac{R_{C2}}{h_{fe} + 1} \quad (5.0.3.16)$$

which, for the values given, yields $R_o = 143.9\Omega$. The output resistance R_{of} of the feed-back amplifier can now be found as

$$R_{of} = R_o(1 + GH) = 143.9(1 + 20.7 \times 11.9) = 35.6K\Omega \quad (5.0.3.17)$$

R_{out} is found by using circuit4 in fig.5.0.3

$$R_{out} = r_{o3} + [R_{of} \parallel (r_{\pi3} + R_{C2})](1 + g_{m3}r_{o3} \frac{r_{\pi3}}{r_{\pi3} + R_{C2}}) \quad (5.0.3.18)$$

$$= 25 + [35.6 \parallel (5.625)][1 + 160 \times 25 \frac{0.625}{5.625}] = 2.19M\Omega \quad (5.0.3.19)$$

thus R_{out} is increased (from r_{o3}) but not by $(1+GH)$

5.0.4. Represent this amplifier in a control system Block Diagram

Solution: figure in fig.5.0.4 represents our control system

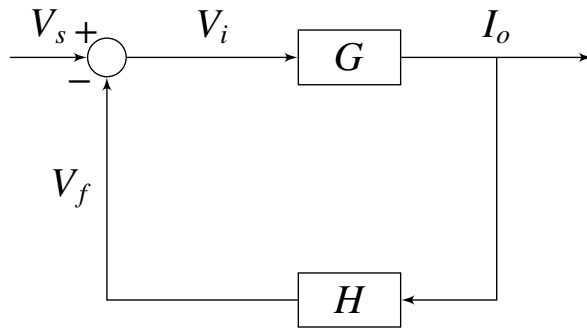


Fig. 5.0.4: block diagram